



<p>Electric Circuits</p> <p>Name the circuit symbols</p>	<p>mrbakerssciencestuff.com</p> <p>1 of 4</p>
<p>Electric Circuits</p> <p>Draw a series circuit</p>	<p>mrbakerssciencestuff.com</p> <p>2 of 4</p>
<p>Electric Circuits</p> <p>Draw a parallel circuit</p>	<p>mrbakerssciencestuff.com</p> <p>3 of 4</p>
<p>Electric Circuits</p> <p>Draw a circuit you could use to measure the electric current through and the potential difference across a component</p>	<p>mrbakerssciencestuff.com</p> <p>4 of 4</p>

Instructions:

- (1) Answer the questions.
- (2) Watch the clip and correct your answers.
- (3) Print out, fold over on dotted line and make into flashcards.
- (4) Use for retrieval quizzes.

