



<p>Series and Parallel Circuits</p> <p>What happens to the total potential difference when you add more cells in series?</p>	<p>mrbakerssciencestuff.com</p> <p>1 of 5</p>
<p>Series and Parallel Circuits</p> <p>Draw a series circuit. When are circuits described as series circuits? Describe the current in a series circuit.</p>	<p>mrbakerssciencestuff.com</p> <p>2 of 5</p>
<p>Series and Parallel Circuits</p> <p>What is the total resistance of a) 2, 5ohm resistors in series? b) 3, 5ohm resistors in series?</p>	<p>mrbakerssciencestuff.com</p> <p>3 of 5</p>
<p>Series and Parallel Circuits</p> <p>Draw a parallel circuit. When are circuits described as parallel circuits? Describe the current in a parallel circuit.</p>	<p>mrbakerssciencestuff.com</p> <p>4 of 5</p>

Instructions:

- (1) Answer the questions.
- (2) Watch the clip and correct your answers.
- (3) Print out, fold over on dotted line and make into flashcards.
- (4) Use for retrieval quizzes.






Series and Parallel Circuits



mrbakerssciencestuff.com

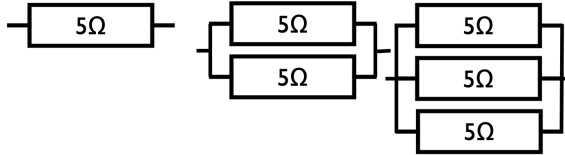What is the total resistance of  
a) 2, 5ohm resistors in parallel?  
b) 3, 5ohm resistors in parallel?



5 of 5

**Instructions:**

- (1) Answer the questions.
- (2) Watch the clip and correct your answers.
- (3) Print out, fold over on dotted line and make into flashcards.
- (4) Use for retrieval quizzes.

